

Time: 2½ hrs.

Marks:75

- Note:
1. All questions are compulsory with internal choice.
  2. Draw neat diagrams wherever necessary.
  3. Figures to the right indicate full marks.

**Q.1 Answer the following (any three) (15)**

(a) Convert :

i)  $(126)_{10}$  to  $(?)_2$

ii)  $(127)_8$  to  $(?)_2$

(b) Solve using 1's complement.

i)  $12 - 10$     ii)  $12 - 13$

(c) Multiply :

i)  $(1101) \times (111)$

ii)  $(1110) \times (110)$

(d) Convert in to BCD :

i)  $(26)_{10}$

ii)  $(52)_{10}$

(e) Perform :

i)  $(1101111) + (111010)$

ii)  $(1111001) - (100101)$

(f) Convert :

i)  $(79)_{10}$  to  $(?)_2$

ii)  $(DB)_{16}$  to  $(?)_2$

**Q.2 Answer the following (any three) (15)**

(a) Explain with the help of circuit diagram how NAND gate is used to create NOT, AND and OR gate?

(b) Describe XNOR and NOR gate with Symbol, Truth table, Boolean expression and Waveform.

(c) Draw the circuit diagram for following Boolean expression.

i.  $\overline{A}C B + \overline{A}\overline{B}C$

ii.  $\overline{B} + B + (\overline{A}B)$

(d) Explain Demorgan's laws.

(e) Draw EXOR gate using NAND gate and then using NOR gate.

(f) Simplify using K-map :  $y = \sum m(1, 2, 9, 10, 11, 14, 15)$

**Q.3 Answer the following (any three) (15)**

(a) Explain half subtractor in detail.

(b) Explain 1 bit comparator.

(c) Simplify using multiplexer :  $y = \sum m(1, 2, 4, 6, 7)$

(d) Explain 4:1 multiplexer.

(e) Design 16:1 multiplexer using 8:1 multiplexer.

(f) Explain full adder in detail.

- Q.4 Answer the following (any three)** (15)
- (a) Explain R-S flip flop with circuit diagram and truth table.
  - (b) Explain J-K flip flop with circuit diagram and truth table.
  - (c) Solve using K map :  $y = \sum m(0, 2, 5, 6, 7, 8, 10, 13, 15)$ .
  - (d) Draw full adder using multiplexer.
  - (e) Draw full subtractor using multiplexer.
  - (f) Explain D flip flop in detail.

- Q.5 Answer the following (any three)** (15)
- (a) Explain 3 bit asynchronous up counter.
  - (b) Design MOD 9 counter.
  - (c) Explain ALU in detail.
  - (d) Design MOD 12 counter.
  - (e) Explain 3 bit asynchronous down counter.
  - (f) Explain serial in serial out shift register.

---X---